

Introduction to Digital Design

Week 2: Switches, Transistors, Logic Gates

Yao Zheng
Assistant Professor
University of Hawai'i at Mānoa
Department of Electrical Engineering

Overview


- Combinational circuit
 - Circuit outputs depend solely on the present combination of the circuit inputs.
- Switches
 - Electronic switches are the basis of binary digital circuits.
 - Three parts: source, output, and control.
- CMOS Transistors
 - Miniaturized switches.
 - NMOS, PMOS.
- Boolean Logic Gates
 - Boolean algebra primer: Boolean expression
 - Basic logic gates: NOT, AND, OR

2


Introduction

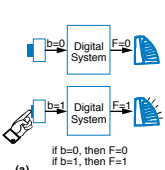2.1


- Let's learn to design digital circuits, starting with a simple form of circuit:
 - **Combinational circuit**
 - Outputs depend solely on the present combination of the circuit inputs' values
 - Vs. sequential circuit: Has "memory" that impacts outputs too



(a)

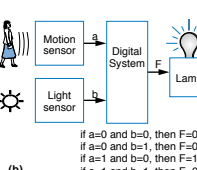

(b)

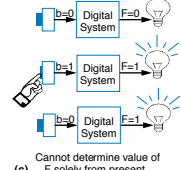

(c)


Note: Slides with animation are denoted with a small red "A" near the animated items

3

Switches

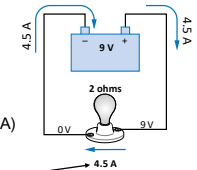2.2

- Electronic switches are the basis of binary digital circuits
 - Electrical terminology
 - **Voltage:** Difference in electric potential between two points (volts, V)
 - Analogous to water pressure
 - **Resistance:** Tendency of wire to resist current flow (ohms, Ω)
 - Analogous to water pipe diameter
 - **Current:** Flow of charged particles (amps, A)
 - Analogous to water flow
 - $V = I * R$ (Ohm's Law)
 - $9V = I * 2\text{ ohms}$
 - $I = 4.5A$






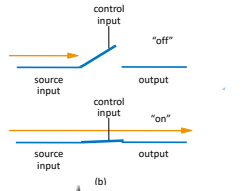
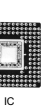
If a 9V potential difference is applied across a 2 ohm resistor, then 4.5 A of current will flow.

4

Switches

- A switch has three parts
 - Source input, and output
 - Current tries to flow from source input to output
 - Control input
 - Voltage that controls whether that current can flow
- The amazing shrinking switch
 - 1930s: Relays
 - 1940s: Vacuum tubes
 - 1950s: Discrete transistor
 - 1960s: Integrated circuits (ICs)
 - Initially just a few transistors on IC
 - Then tens, hundreds, thousands...




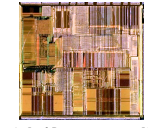





quarter
(to see the relative size)

5

Moore's Law

- IC capacity doubling about every 18 months for several decades
 - Known as "Moore's Law" after Gordon Moore, co-founder of Intel
 - Predicted in 1965 predicted that components per IC would double roughly every year or so
 - Book cover depicts related phenomena
 - For a particular number of transistors, the IC area shrinks by half every 18 months
 - Consider how much shrinking occurs in just 10 years (try drawing it)
 - Enables incredibly powerful computation in incredibly tiny devices
 - Today's ICs hold *billions* of transistors
 - The first Pentium processor (early 1990s) needed only 3 million


An Intel Pentium processor IC having millions of transistors

6

The CMOS Transistor

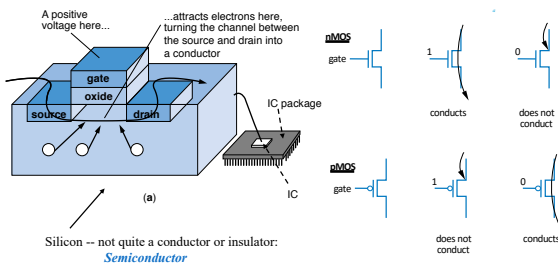
2.3

- CMOS transistor
 - Basic switch in modern ICs



7


CMOS Transistor Analogy

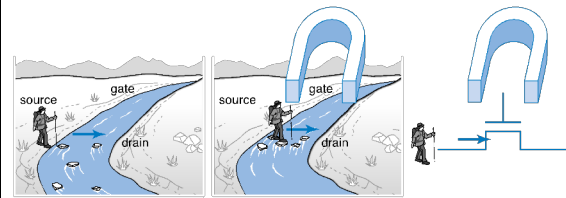

8

Boolean Logic Gates Building Blocks for Digital Circuits (Because Switches are Hard to Work With)

2.4

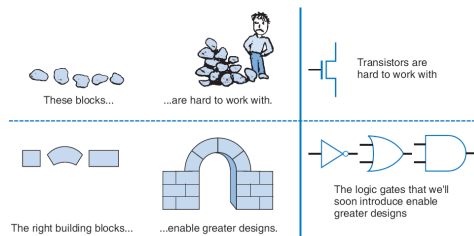

- "Logic gates" are better digital circuit building blocks than switches (transistors)
 - Why?...

9

Boolean Algebra and its Relation to Digital Circuits

- To understand the benefits of "logic gates" vs. switches, we should first understand Boolean algebra
- "Traditional" algebra
 - Variables represent real numbers (x, y)
 - Operators operate on variables, return real numbers ($2.5 \cdot x + y - 3$)

Boolean Algebra

- Variables represent 0 or 1 only
- Operators return 0 or 1 only
- Basic operators
 - AND: $a \text{ AND } b$ returns 1 only when both $a=1$ and $b=1$
 - OR: $a \text{ OR } b$ returns 1 if either (or both) $a=1$ or $b=1$
 - NOT: $\text{NOT } a$ returns the opposite of a (1 if $a=0$, 0 if $a=1$)

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0

10

Boolean Algebra and its Relation to Digital Circuits

- Developed mid-1800's by George Boole to formalize human thought
 - Ex: "I'll go to lunch if Mary goes OR John goes, AND Sally does not go."
 - Let F represent my going to lunch (1 means I go, 0 I don't go)
 - Likewise, m for Mary going, j for John, and s for Sally
 - Then $F = (m \text{ OR } j) \text{ AND NOT}(s)$
 - Nice features
 - Formally evaluate
 - $m=1, j=0, s=1 \rightarrow F = (1 \text{ OR } 0) \text{ AND NOT}(1) = 1 \text{ AND } 0 = 0$
 - Formally transform
 - $F = (m \text{ AND NOT}(s)) \text{ OR } (j \text{ AND NOT}(s))$
 - Looks different, but same function
 - We'll show transformation techniques soon
 - Formally prove
 - Prove that if Sally goes to lunch ($s=1$), then I don't go ($F=0$)
 - $F = (m \text{ OR } j) \text{ AND NOT}(1) = (m \text{ OR } j) \text{ AND } 0 = 0$

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0

11

Evaluating Boolean Equations

- Evaluate the Boolean equation $F = (a \text{ AND } b) \text{ OR } (c \text{ AND } d)$ for the given values of variables a, b, c , and d :

- Q1: $a=1, b=1, c=1, d=0$.
 - Answer: $F = (1 \text{ AND } 1) \text{ OR } (1 \text{ AND } 0) = 1 \text{ OR } 0 = 1$.
- Q2: $a=0, b=1, c=0, d=1$.
 - Answer: $F = (0 \text{ AND } 1) \text{ OR } (0 \text{ AND } 1) = 0 \text{ OR } 0 = 0$.
- Q3: $a=1, b=1, c=1, d=1$.
 - Answer: $F = (1 \text{ AND } 1) \text{ OR } (1 \text{ AND } 1) = 1 \text{ OR } 1 = 1$.

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0

12

Converting to Boolean Equations

- Convert the following English statements to a Boolean equation
 - Q1. a is 1 and b is 1.
 - Answer: $F = a \text{ AND } b$
 - Q2. either of a or b is 1.
 - Answer: $F = a \text{ OR } b$
 - Q3. a is 1 and b is 0.
 - Answer: $F = a \text{ AND NOT}(b)$
 - Q4. a is not 0.
 - Answer:
 - (a) Option 1: $F = \text{NOT}(\text{NOT}(a))$
 - (b) Option 2: $F = a$


13

Converting to Boolean Equations

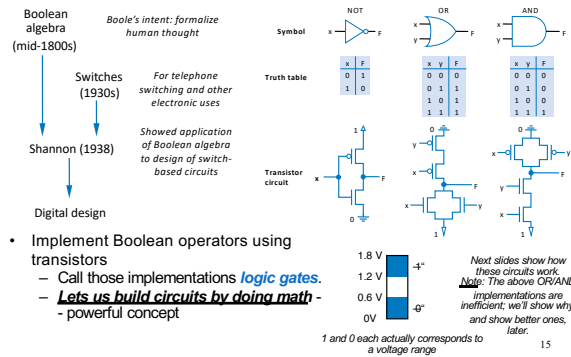- Q1. A fire sprinkler system should spray water if high heat is sensed and the system is set to enabled.
 - Answer: Let Boolean variable h represent "high heat is sensed," e represent "enabled," and F represent "spraying water." Then an equation is: $F = h \text{ AND } e$.
- Q2. A car alarm should sound if the alarm is enabled, and either the car is shaken or the door is opened.
 - Answer: Let a represent "alarm is enabled," s represent "car is shaken," d represent "door is opened," and F represent "alarm sounds." Then an equation is: $F = a \text{ AND } (s \text{ OR } d)$.
 - (a) Alternatively, assuming that our door sensor d represents "door is closed" instead of open (meaning d=1 when the door is closed, 0 when open), we obtain the following equation: $F = a \text{ AND } (s \text{ OR NOT}(d))$.


14

Relating Boolean Algebra to Digital Design




15

NOT gate

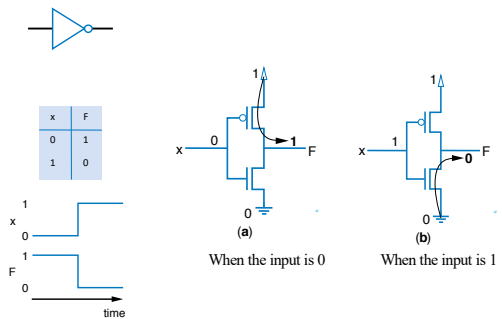

16

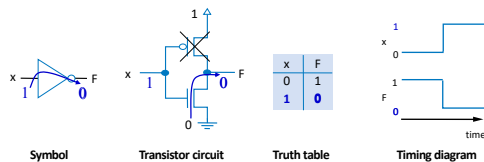
Relating a Logic Gate Symbol, Circuit, Truth Table, and Timing Diagram



Setting x to 1 causes F to be 0

17

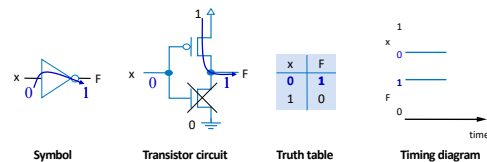
Relating a Logic Gate Symbol, Circuit, Truth Table, and Timing Diagram



Setting x to 0 causes F to be 1


18

OR gate

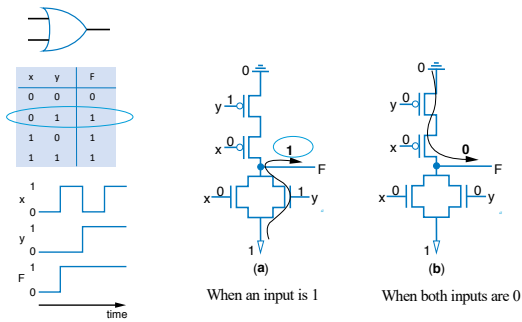


19

AND gate

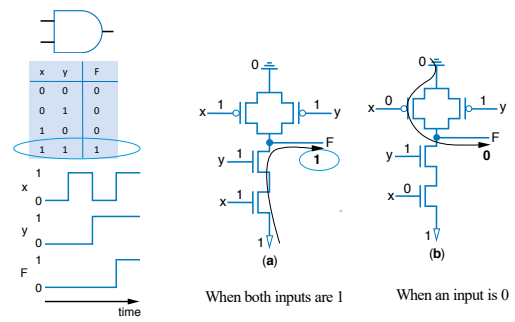

20

Building Circuits Using Gates

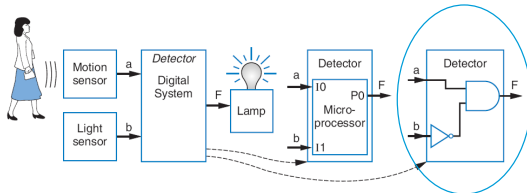

- Recall Chapter 1 motion-in-dark example
 - Turn on lamp ($F=1$) when motion sensed ($a=1$) and no light ($b=0$)
 - $F = a \text{ AND NOT}(b)$
 - Build using logic gates, AND and NOT, as shown
 - We just built our first digital circuit!

21

Example: Converting a Boolean Equation to a Circuit of Logic Gates

Start from the output, work back towards the inputs

- Q: Convert the following equation to logic gates:


$$F = a \text{ AND NOT}(b \text{ OR NOT}(c))$$



22

Example: Converting a Boolean Equation to a Circuit of Logic Gates

[Video](#)

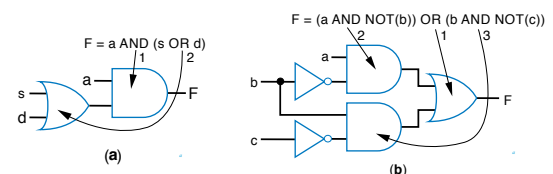

Start from the output, work back towards the inputs


24

More examples

[Video](#)

25

Using gates with more than 2 inputs

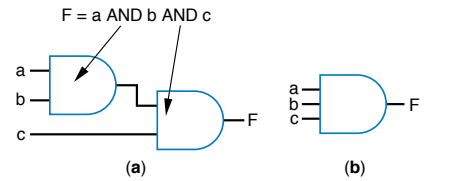

Can think of as $\text{AND}(a,b,c)$

26


Example: Seat Belt Warning Light System

- Design circuit for warning light
- Sensors
 - $s=1$: seat belt fastened
 - $k=1$: key inserted

- Capture Boolean equation
 - seat belt not fastened, and key inserted

- Convert equation to circuit

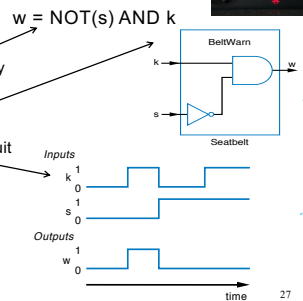- Timing diagram illustrates circuit behavior
 - We set inputs to any values
 - Output set according to circuit



27

Example: Seat Belt Warning Light System

[Video](#)


28

Gates vs. switches

Notice

- Boolean algebra enables easy capture as equation and conversion to circuit

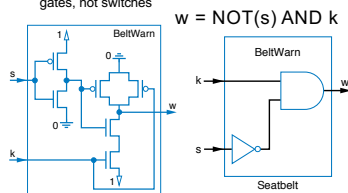
- How design with switches?
- Of course, logic gates are built from switches, but we think at level of logic gates, not switches




29

More examples: Seat belt warning light extensions

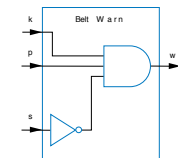- Only illuminate warning light if person is in the seat ($p=1$), and seat belt not fastened and key inserted
- $w = p \text{ AND } \text{NOT}(s) \text{ AND } k$




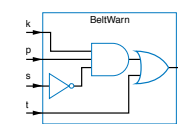- Given $t=1$ for 5 seconds after key inserted. Turn on warning light when $t=1$ (to check that warning lights are working)
- $w = (p \text{ AND } \text{NOT}(s) \text{ AND } k) \text{ OR } t$



30

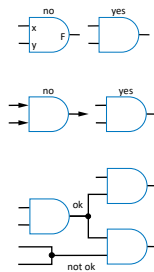Some Gate-Based Circuit Drawing Conventions



31

Summary

- Combinational circuit
 - Circuit outputs depend solely on the present combination of the circuit inputs.
- Switches
 - Electronic switches are the basis of binary digital circuits.
 - Three parts: source, output, and control.
- CMOS Transistors
 - Miniaturized switches.
 - NMOS, PMOS.
- Boolean Logic Gates
 - Boolean algebra primer: Boolean expression
 - Basic logic gates: NOT, AND, OR

32